 


UNIT – I

REGISTER TRANSFER AND MICROOPERATIONS

Components of Computer System




TOPICS

 
- 1. Register Transfer Language**
- 2. Register Transfer**
- 3. Bus and Memory Transfers**
- 4. Arithmetic Microoperations**
- 5. Logic Microoperations**
- 6. Shift Microoperations**
- 7. Arithmetic Logic Shift Unit**

About Register Representation


- Register is a storage device which store one or more bits




(a) Register R

 

(b) Showing individual bits

 

(c) Numbering of bits

 

(d) Divided into two parts

Definition

- BUS: In computer architecture, a bus is a communication system that transfers data between components inside a computer, or between computers.
- Digital System: An interconnection of hardware modules that do a certain task on the information.
- Registers + Operations performed on the data stored in them = Digital Module
- Modules are interconnected with common data and control paths to form a digital computer system

1. Register Transfer Language

- Microoperations: operations executed on data stored in one or more registers.
- For any function of the computer, a sequence of microoperations is used to describe it
- The result of the operation may be:
 - replace the previous binary information of a register or
 - transferred to another register

1. Register Transfer Language ^{cont.}

- The internal hardware organization of a digital computer is defined by specifying:
 - The set of registers it contains and their function
 - The sequence of microoperations performed on the binary information stored in the registers
 - The control that initiates the sequence of microoperations
- Registers + Microoperations Hardware + Control Functions = Digital Computer

1 Register Transfer Language ^{cont.}

- Register Transfer Language (RTL) : a symbolic notation to describe the micro operation transfers among registers

So the next thing is

- Define symbols for various types of microoperations,
- Describe the hardware that implements these microoperations

2. Register Transfer

- Computer registers are designated by capital letters.
- Few specific registers are
 - R1: processor register
 - MAR: Memory Address Register (holds an address for a memory unit)
 - PC: Program Counter
 - IR: Instruction Register
 - SR: Status Register

2. Register Transfer ^{cont.}

- Information transfer from one register to another is described by a *replacement operator*:

$$\mathbf{R2 \leftarrow R1}$$

- This statement denotes a transfer of the content of register R1 into register R2
- The transfer happens in one clock cycle
- We are assuming that the circuits are available from the outputs of the source register to the inputs of the destination register, and that the destination register has a parallel load capability

2. Register Transfer ^{cont.}

- Conditional transfer occurs only under a control condition.
- Representation of a (conditional) transfer

$$P: \quad R2 \leftarrow R1$$


- The content of R1 is transferred into R2 only if P is 1

2 Register Transfer cont.


Basic Symbols for Register Transfers		
Symbol	Description	Examples
Letters & numerals	Denotes a register	MAR, R2
Parenthesis ()	Denotes a part of a register	R2(0-7), R2(L)
Arrow \leftarrow	Denotes transfer of information	R2 \leftarrow R1
Comma ,	Separates two microoperations	R2 \leftarrow R1, R1 \leftarrow R2

 2. Register Transfer cont.

Hardware implementation of a controlled transfer: $P: R2 \leftarrow R1$



(a) Block diagram


 


(b) Timing diagram

3 Bus and Memory Transfers

- A Common Bus System is a scheme for transferring information between registers in a multiple-register configuration
- A bus: set of common lines, one for each bit of a register, through which binary information is transferred one at a time
- Control signals determine which register is selected by the bus during each particular register transfer

3 Bus and Memory Transfers

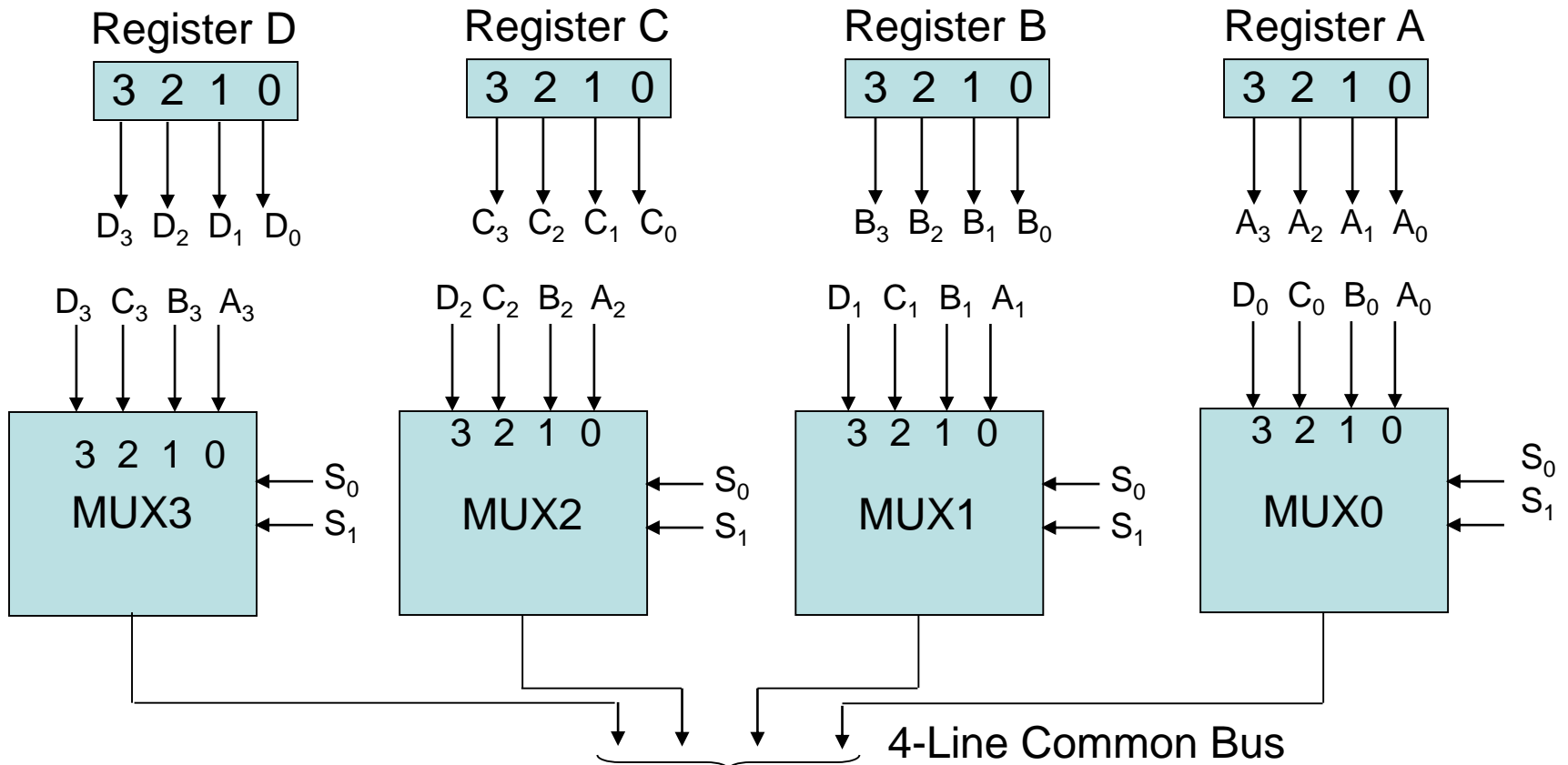 

3 Bus and Memory Transfers

Bus System for four registers


S_1	S_0	Register selected
0	0	A
0	1	B
1	0	C
1	1	D

3. Bus and Memory Transfers

- We write: $R2 \leftarrow C$ to symbolize that the content of register C is *loaded into* the register $R2$ using the common system bus
- It is equivalent to: $BUS \leftarrow C$, (select C)
 $R2 \leftarrow BUS$ (Load $R2$)

 
3. Bus and Memory Transfers: Three-State Bus Buffers

- A bus system can be constructed with three-state buffer gates instead of multiplexers
- A three-state buffer is a digital circuit that exhibits three states: logic-0, logic-1, and high-impedance (Hi-Z)




Three-State Buffer

 3. Bus and Memory Transfers: Three-State Bus Buffers ^{cont.}



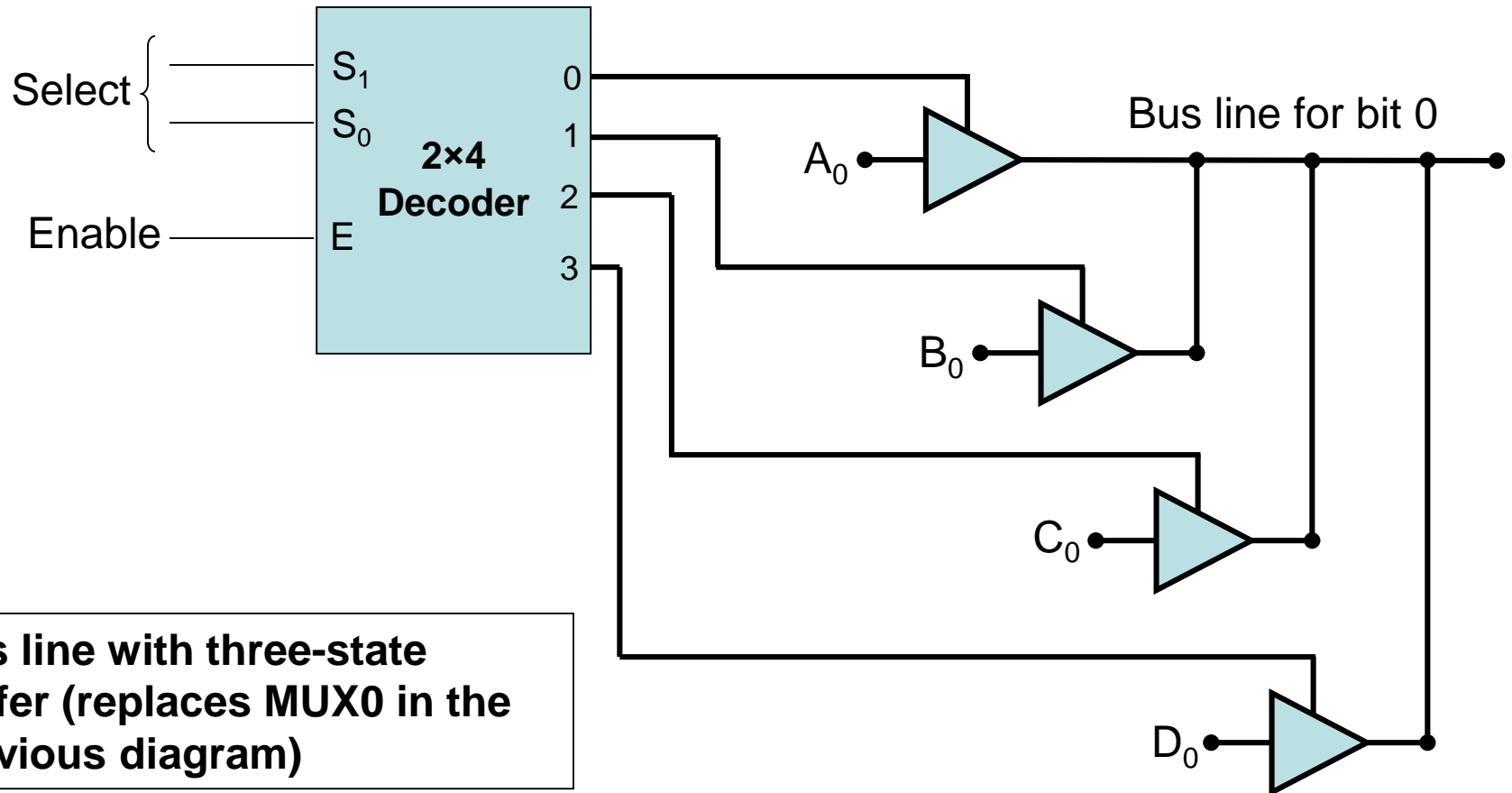3. Bus and Memory Transfers: Three-State Bus Buffers cont.



3. Bus and Memory Transfers:


Memory Transfer

- Memory read : Transfer from memory
- Memory write : Transfer to memory
- Data being read or written is called a memory word
- It is necessary to specify the address of M when writing /reading memory
- This is done by enclosing the address in square brackets following the letter M
- Example: M[0016] : the memory contents at address 0x0016

3. Bus and Memory Transfers: Memory Transfer ^{cont.}

- Assume that the address of a memory unit is stored in a register called the Address Register AR
- Lets represent a Data Register with DR,
then:
 - Read: $DR \leftarrow M[AR]$
 - Write: $M[AR] \leftarrow DR$

 3. Bus and Memory Transfers: Memory Transfer cont.



Types of Microoperations

- The microoperations most often classified into four categories:
 - 1. Register transfer microoperations**
 - 2. Arithmetic microoperations (on numeric data stored in the registers)**
 - 3. Logic microoperations (bit manipulations on non-numeric data)**
 - 4. Shift microoperations**

4. Arithmetic Microoperations ^{cont.}

- The basic arithmetic microoperations are: addition, subtraction, increment, decrement, and shift
- Addition Microoperation:

$$\mathbf{R3 \leftarrow R1 + R2}$$

- Subtraction Microoperation:

$$\mathbf{R3 \leftarrow R1 - R2 \text{ or :}}$$

$$\mathbf{R3 \leftarrow R1 + \overline{R2} + 1}$$

1's complement

4. Arithmetic Microoperations ^{cont.}

- One's Complement Microoperation:

$$R2 \leftarrow \overline{R2}$$

- Two's Complement Microoperation:

$$R2 \leftarrow R2+1$$

- Increment Microoperation:

$$R2 \leftarrow R2+1$$

- Decrement Microoperation:

$$R2 \leftarrow R2-1$$

Half Adder/Full Adder


Half Adder

x	y	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$c = xy$$


$$s = xy' + x'y$$

$$= x \oplus y$$

 

Full Adder

x	y	C_{n-1}	C_n	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


$$C_n = xy + xC_{n-1} + yC_{n-1}$$

$$= xy + (x \oplus y)C_{n-1}$$


$$s = x'y'C_{n-1} + x'yc'_{n-1} + xy'c'_{n-1} + xyc_{n-1}$$
 
$$= x \oplus y \oplus C_{n-1} = (x \oplus y) \oplus C_{n-1}$$



4. Arithmetic Microoperations


Binary Adder

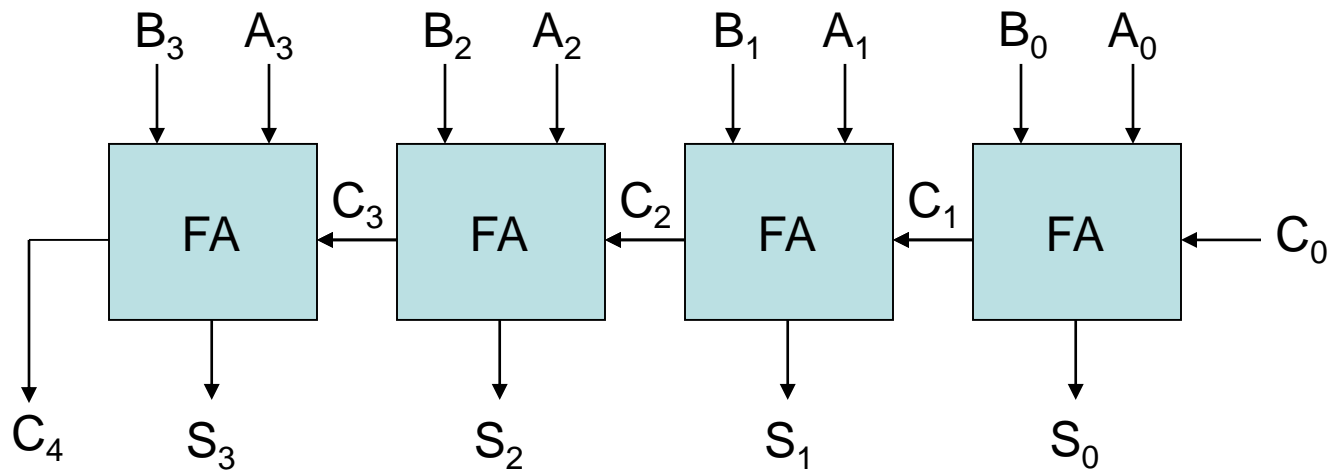

**4-bit binary adder
(connection of FAs)**

4. Arithmetic Microoperations


Binary Adder-Subtractor

 

4-bit adder-subtractor

4. Arithmetic Microoperations

Binary Incrementer

 

4-bit Binary Incrementer

4. Arithmetic Microoperations

Binary Incrementer

- Binary Incrementer can also be implemented using a counter
- A binary decrementer can be implemented by adding 1111 to the desired register each time!


5. Logic Microoperations

The four basic microoperations

OR Microoperation

- Symbol: \vee , $+$

- Gate:

 

- Example: $100110_2 \vee 1010110_2 = 1110110_2$

5. Logic Microoperations


The four basic microoperations

cont.

AND Microoperation

- Symbol: \wedge

- Gate:

 

- Example: $100110_2 \wedge 1010110_2 = 0000110_2$


5. Logic Microoperations

The four basic microoperations

cont.

Complement (NOT) Microoperation

- Symbol: $\bar{\quad}$

 

- Gate:

- Example: $\overline{1010110}_2 = 0101001_2$


5. Logic Microoperations

The four basic microoperations

cont.

XOR (Exclusive-OR) Microoperation

- Symbol: \oplus

 

- Gate:

- Example: $100110_2 \oplus 1010110_2 = 1110000_2$


5. Logic Microoperations

Other Logic Microoperations cont.

NAND Microoperation

- Symbols: \wedge and $\bar{\quad}$

- Gate:

 

- Example: $100110_2 \wedge 1010110_2 = 1111001_2$


5. Logic Microoperations

Other Logic Microoperations cont.

NOR Microoperation

- Symbols: \vee and $\bar{}$

- Gate:

 

- Example: $100110_2 \vee 1010110_2 = 0001001_2$

5. Logic Microoperations

Other Logic Microoperations cont.

Set (Preset) Microoperation

- Force all bits into 1's by ORing them with a value in which all its bits are being assigned to logic-1
- Example: $100110_2 \vee 111111_2 = 111111_2$

Clear (Reset) Microoperation

- Force all bits into 0's by ANDing them with a value in which all its bits are being assigned to logic-0
- Example: $100110_2 \wedge 000000_2 = 000000_2$


5. Logic Microoperations

Hardware Implementation

- The hardware implementation of logic microoperations requires that logic gates be inserted for each bit or pair of bits in the registers to perform the required logic function
- Most computers use only four (AND, OR, XOR, and NOT) from which all others can be derived.

5. Logic Microoperations

Hardware Implementation cont.

 

S_1	S_0	Output	Operation
0	0	$E = A \oplus B$	XOR
0	1	$E = A \vee B$	OR
1	0	$E = A \wedge B$	AND
1	1	$E = A$	Complement

This is for one bit i


6. Shift Microoperations

- Used for serial transfer of data
- The contents of the register can be shifted to the left or to the right
- As being shifted, the first flip-flop receives its binary information from the serial input
- Three types of shift: Logical, Circular, and Arithmetic

6. Shift Microoperations ^{cont.}

Symbolic designation	Description
$R \leftarrow \text{shl } R$	Shift-left register R
$R \leftarrow \text{shr } R$	Shift-right register R
$R \leftarrow \text{cil } R$	Circular shift-left register R
$R \leftarrow \text{cir } R$	Circular shift-right register R
$R \leftarrow \text{ashl } R$	Arithmetic shift-left R
$R \leftarrow \text{ashr } R$	Arithmetic shift-right R


6. Shift Microoperations ^{cont.}

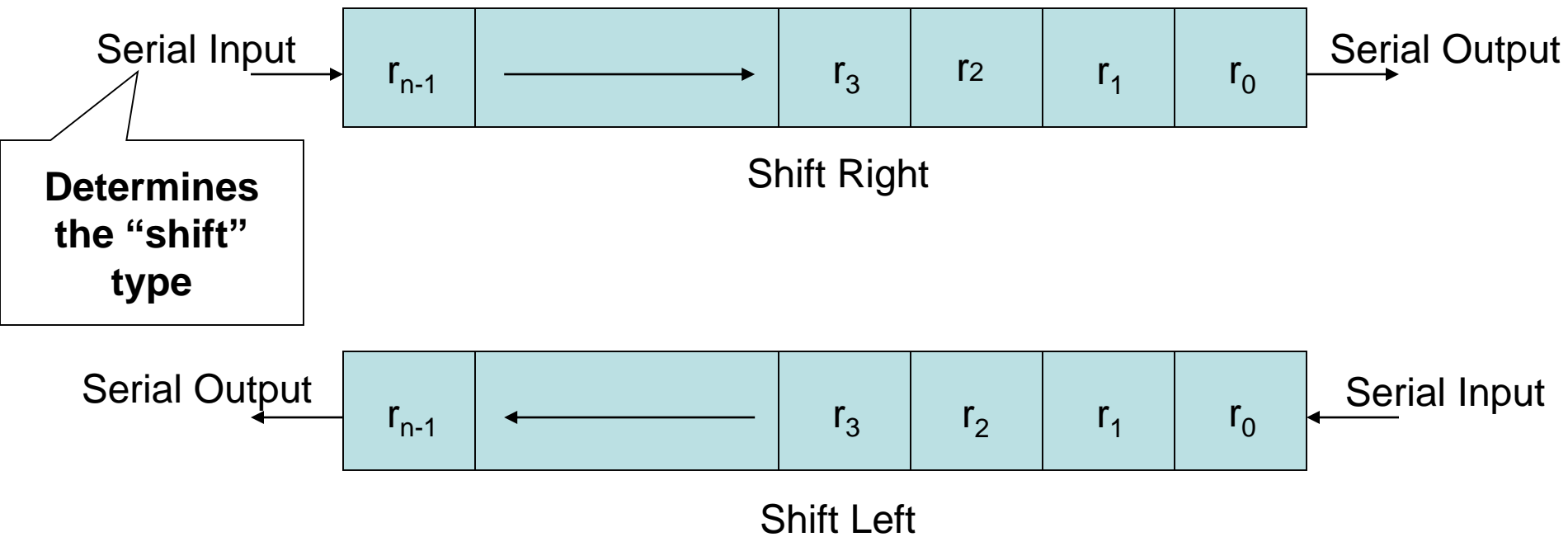

**Note that the bit r_i is the bit at position (i) of the register

 6. Shift Microoperations: Logical Shifts


- Transfers 0 through the serial input
- Logical Shift Right: $R1 \leftarrow shr R1$
The same
- Logical Shift Left: $R2 \leftarrow shl R2$
The same



Logical Shift Left

 6. Shift Microoperations: Circular Shifts (Rotate Operation)

- Circulates the bits of the register around the two ends without loss of information
- Circular Shift Right: $R1 \leftarrow \text{cir } R1$
The same
- Circular Shift Left: $R2 \leftarrow \text{cil } R2$
The same



Circular Shift Left


6. Shift Microoperations

Arithmetic Shifts

- Shifts a signed binary number to the left or right
- An arithmetic shift-left multiplies a signed binary number by 2: ashl (00100): 01000
- An arithmetic shift-right divides the number by 2
 ashr (00100) : 00010


6. Shift Microoperations

Arithmetic Shifts ^{cont.}

 

Sign
Bit

Arithmetic Shift Right

 

Sign
Bit

Arithmetic Shift Left

6. Shift Microoperations

Arithmetic Shifts ^{cont.}


- Arithmetic Shift Right operation divides the number by 2.
- Arithmetic Shift left operation multiplies the number by 2.
- Overflow means whether we required extra bit or not
- Overflow may occur in Arithmetic Left Shift operation if the sign bit has changed.

6. Shift Microoperations

Arithmetic Shifts cont.

- An overflow flip-flop V_s can be used to detect an arithmetic shift-left overflow


$$V_s = R_{n-1} \oplus R_{n-2}$$

 

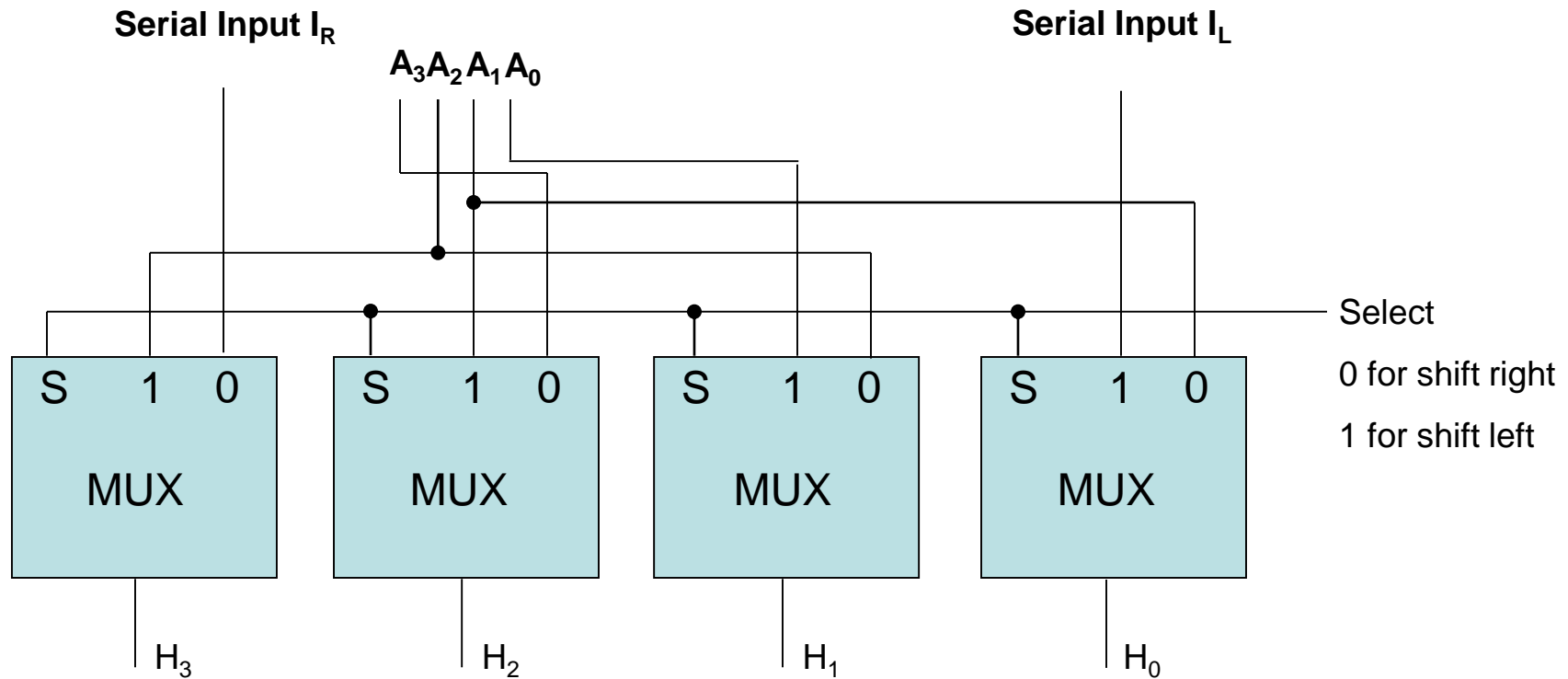6. Shift Microoperations

Hardware Implementation cont.

- Implement of shift operation with a combinational circuit




4-bit Combinational Circuit Shifter

Select	Output			
	H ₃	H ₂	H ₁	H ₀
0	I _R	A ₀	A ₁	A ₂
1	A ₁	A ₂	A ₃	I _L

7. Arithmetic Logic Shift Unit

- Instead of having individual registers performing the microoperations directly, computer systems employ a number of storage registers connected to a common operational unit called an Arithmetic Logic Unit (**ALU**)

7. Arithmetic Logic Shift Unit cont.

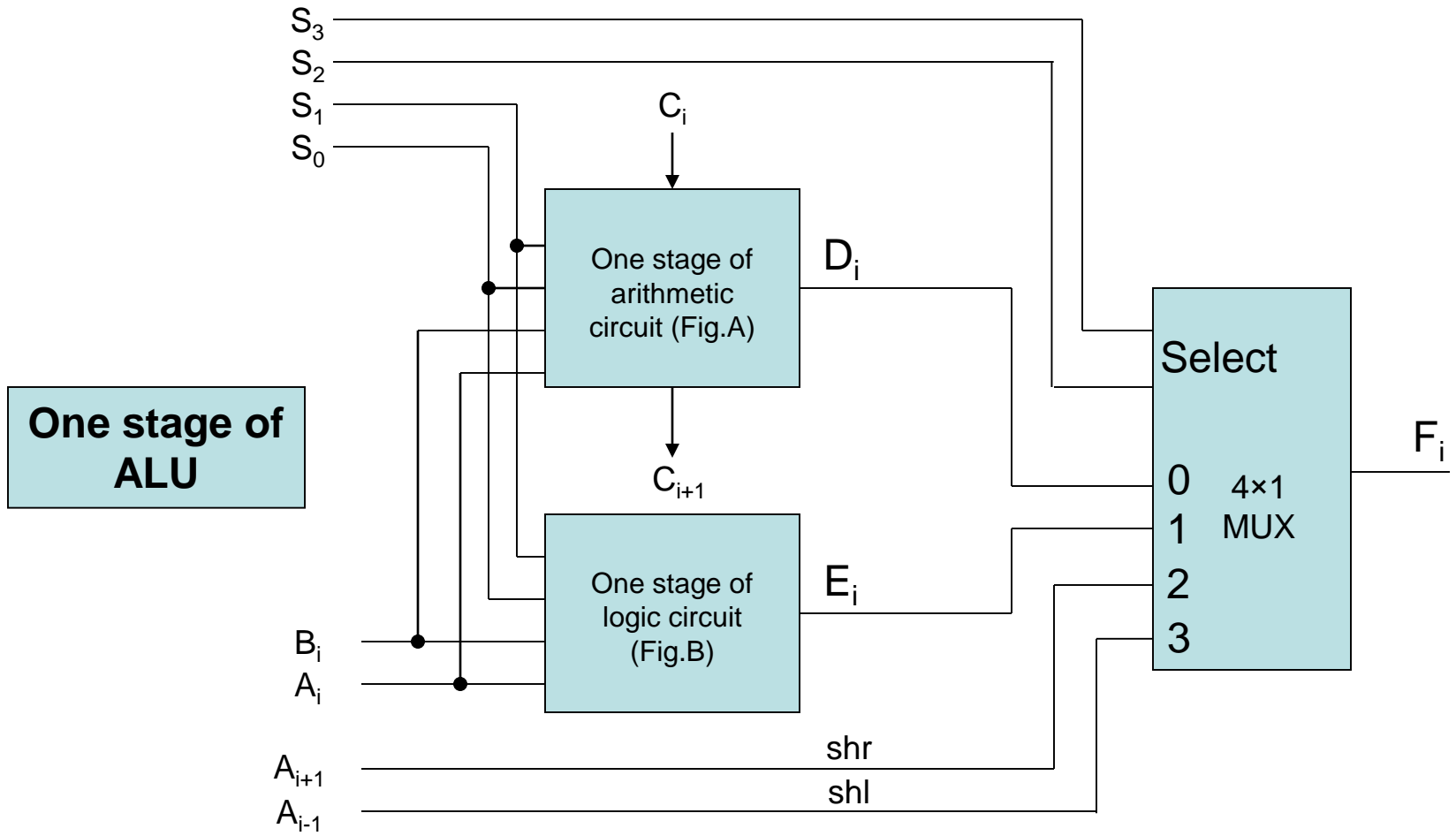

7. Arithmetic Logic Shift Unit ^{cont.}

Operation select					Operation	Function
S_3	S_2	S_1	S_0	C_{in}		
0	0	0	0	0	$F = A$	Transfer A
0	0	0	0	1	$F = A + 1$	Increment A
0	0	0	1	0	$F = A + B$	Addition
0	0	0	1	1	$F = A + B + 1$	Add with carry
0	0	1	0	0	$F = A + \bar{B}$	Subtract with borrow
0	0	1	0	1	$F = A + \bar{B} + 1$	Subtraction
0	0	1	1	0	$F = A - 1$	Decrement A
0	0	1	1	1	$F = A$	Transfer A
0	1	0	0	x	$F = A \wedge B$	AND
0	1	0	1	x	$F = A \vee B$	OR
0	1	1	0	x	$F = A \oplus B$	XOR
0	1	1	1	x	$F = \bar{A}$	Complement A
1	0	x	x	x	$F = \text{shr } A$	Shift right A into F
1	1	x	x	x	$F = \text{shl } A$	Shift left A into F

Assignment - 1.

1. What is the range of unsigned numbers that can be represented in 4 bits?
2. What is the range of signed numbers that can be represented in 4 bits?
3. Example: Assume $R1=11001110$,

then:

Arithmetic shift right once ,Arithmetic shift right twice,
Arithmetic shift left once, Arithmetic shift left twice,
Logical shift right once, Logical shift left once,
Circular shift right once, Circular shift left once

Assignment - 1

- Example: Assume $R1=11001110$, then:
 - Arithmetic shift right once : $R1 = 11100111$
 - Arithmetic shift right twice : $R1 = 11110011$
 - Arithmetic shift left once : $R1 = 10011100$
 - Arithmetic shift left twice : $R1 = 00111000$
 - Logical shift right once : $R1 = 01100111$
 - Logical shift left once : $R1 = 10011100$
 - Circular shift right once : $R1 = 01100111$
 - Circular shift left once : $R1 = 10011101$